

Week 17 (1/6/03)

Icosahedron of resistors

Each edge of an icosahedron is a 1Ω resistor. Find the effective resistance between two adjacent vertices. (An icosahedron consists of 20 equilateral triangles. It has 12 vertices and 30 edges, with 5 edges meeting at each vertex.)